

# Testing and Verification of VLSI EE709

Mohit  
20D070052

April 2023



## 1 Student Details

Name: Mohit  
Roll No: 20D070052

## 2 Question 1

### 2.1 Calculating the product of sums formula (CNF) which describes this network.

CNF (product of sums formula) form is given below :

$$K = (\overline{AB} + \overline{BC}) \oplus (\overline{BC} + \overline{CD})$$

As it is XOR, we can also write it as-

$$\begin{aligned} & (\overline{AB} + \overline{BC}) \oplus (\overline{BC} + \overline{CD}) \\ & ((\overline{A} + \overline{B}) + (\overline{B} + \overline{C})) \oplus ((\overline{B} + \overline{C}) + (\overline{C} + \overline{D})) \\ & (\overline{A} + \overline{B} + \overline{C}) \oplus (\overline{B} + \overline{C} + \overline{D}) \\ & \overline{A}BCD + ABC\overline{D} \\ & BC(\overline{A}D + A\overline{D}) \\ & B.C.(A + D).(\overline{A} + \overline{D}) \end{aligned}$$

CNF is -

$$K = B.C.(A + D).(\overline{A} + \overline{D})$$

### 2.2 Using the minisat solver, find an input assignment such that the output K is 0

To solve the above, we will find the negation CNF form of the above to get

$$\overline{K} = \overline{ABCD + ABC\overline{D}}$$

$$\overline{K} = (A + \overline{B} + \overline{C} + \overline{D}).(\overline{A} + \overline{B} + \overline{C} + D)$$

This CNF form in the minisat solver with the following code:

```
c
c  nvars nclauses
p cnf 4 2
c
c  -2 means (~x2), 2 means x2
c  A = x1, B = x2, C = x3, D = x4
```

```

c
c   x1 + x2 + x3 + ~x4
1 2 3 -4 0
c
c   ~x1 + x2 + x3 + x4
-1 2 3 4 0

```

Result -  
 SAT  
 -1 -2 -3 -4 0

The equation  $K = 0$  can be satisfied using -

$$\overline{A}, \overline{B}, \overline{C}, \overline{D}$$

which is, as given by SAT solver

$$A = 0, B = 0, C = 0, D = 0$$

### 2.3 Using the minisat solver, find an input assignment such that the output K is 1.

We insert the above CNF form of K in the minisat solver with the following code:

$$K = B.C.(A + D).(\overline{A} + \overline{D})$$

```

c
c   nvars nclauses
p cnf 4 4
c.
c   -2 means (~x2), 2 means x2
c   A = x1, B = x2, C = x3, D = x4
c
c   x2
2 0
c
c   x3
3 0
c

```

```

c    x1 + x4
1 4 0
c
c    (~x1) + (~x4)
-1 -4 0

```

```

Result - SAT
-1 2 3 4 0

```

The equation  $K = 0$  can be satisfied using SAT solver -

$$\overline{A}, B, C, D$$

which is,

$$A = 0, B = 1, C = 1, D = 1$$

## 3 Question 2

### 3.1 Method

Suppose the machine starts in the state  $P = Q = R = S = 1$ . Using minisat, finding a sequence of input values at  $X$  which will take the machine to the state  $P = Q = R = S = 0$ .

Let  $P(k), Q(k), R(k), S(k)$  be the state variables at time  $k$ . Also, let  $X(k)$  be the input at time  $k$ . Note that  $Y(k) = P(k) \oplus S(k)$ .

To solve the problem, we observe:

1. At  $k = 0, P(k) = Q(k) = R(k) = S(k) = 1$ . That is, at  $k = 0$ , the following function is true.

$$C_0 = P(0).Q(0).R(0).S(0)$$

2. At some time  $N$ , we want  $P(N) = Q(N) = R(N) = S(N) = 0$ . That is, at time  $N$ , the following function is true:

$$D_N = \overline{P(N)} \cdot \overline{Q(N)} \cdot \overline{R(N)} \cdot \overline{S(N)}$$

Further, we have -

$$P(k+1) = X(k) \oplus P(k) \oplus S(k)$$

$$Q(k+1) = P(k)$$

$$R(k+1) = Q(k)$$

$$S(k+1) = R(k)$$

To find the solution, we proceed as follows. At any  $k > 0$ , the relation between the state variables at time  $k$  and those at time  $k-1$  is described by the function

$$\begin{aligned} \phi_k = & (P(k) = X(k-1) \oplus P(k-1) \oplus S(k-1)) \\ & \cdot (Q(k) = P(k-1)) \\ & \cdot (R(k) = Q(k-1)) \\ & \cdot (S(k) = R(k-1)) \end{aligned}$$

Thus, to see if it possible to find an input sequence which takes us to state  $P(N) = Q(N) = R(N) = S(N) = 0$  at some time  $N > 0$ , we build the following function (for  $N = 1, 2, \dots, 15$ )<sup>1</sup>.

$$\Theta_N = C_0 \cdot \phi_1 \cdot \phi_2 \dots \phi_N \cdot D_N$$

and check if it is satisfiable.

## 3.2 Solution

We define the above-mentioned variables at different N and find the CNF forms of each of the above. Next, we keep on adding our code for  $N = 1, 2, 3, 4, \dots$  and check the resultant output for each case until we get our desired output as  $P(N)=Q(N)=R(N)=S(N)=0$ .

## 3.3 Code

```
c  nvars nclauses
p cnf 10 22
c   -2 means (~x2), 2 means x2
c   X(0)=1, P(0)=2, Q(0)=3, R(0)=4, S(0)=5
c   X(1)=6, P(1)=7, Q(1)=8, R(1)=9, S(1)=10
```

```

c   At time N=0 (phi_0)
c   P(0)
2 0
c   Q(0)
3 0
c   R(0)
4 0
c   S(0)
5 0
c   At time N=1 (phi_1)
c   ~X(0) ~P(0) ~S(0) P(1)
-1 -2 -5 7 0
c   X(0) P(0) ~S(0) P1
1 2 -5 7 0
c   X(0) ~P(0) S(0) P(1)
1 -2 5 7 0
c   ~X(0) P(0) S(0) P(1)
-1 2 5 7 0
c   X(0) ~P(0) ~S(0) ~P(1)
1 -2 -5 -7 0
c   ~X(0) P(0) ~S(0) ~P1(1)
-1 2 -5 -7 0
c   ~X(0) ~P(0) S(0) ~P(1)
-1 -2 5 -7 0
c   X(0) P(0) S(0) ~P(1)
1 2 5 -7 0
c   Q(1) + ~P(0)
8 -2 0
c   ~Q(1) + P(0)
-8 2 0
c   R(1) + ~Q(0)
9 -3 0
c   ~R(1) + Q(0)
-9 3 0
c   S(1) + ~R(0)
10 -4 0
c   ~S(1) R(0)
-10 4 0

```

```

c    n=N=1 (D_n)
c    ~P(1)
-7 0
c    ~Q(1)
-8 0
c    ~R(1)
-9 0
c    ~S(1)
-10 0

```

There is no values satisfying the above equation as we get its output as **Output for N = 1 UNSAT**

Similarly, we write code for N = 2,3,4 and observe the outputs for then:

**Output for N = 2 UNSAT**

**Output for N = 3 UNSAT**

For N=4, the following values are satisfying the conditions  $P(N)=Q(N)=R(N)=S(N)=0$ .

SAT

-1 2 3 4 5 6 -7 8 9 10 11 -12 -13 14 15 16 -17 -18 -19 20 -21 -22 -23 -24 -25 0

## 4 Conclusion

Hereby the assignment is completed using the minisat solver.